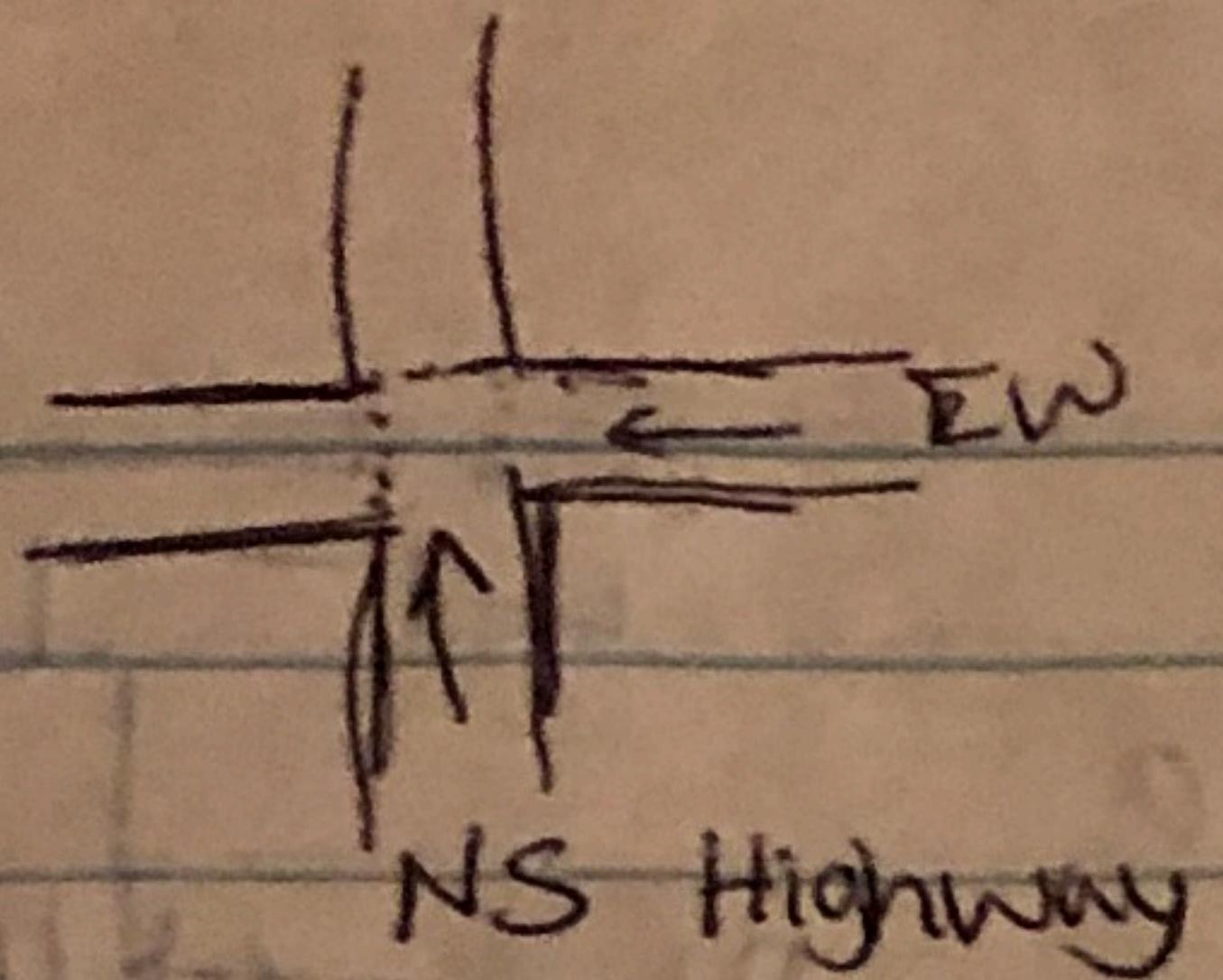



Rishi Sheth
12/18/23

Bonus Assignment 2



R_{NS}, Y_{NS}, G_{NS} } outputs
 R_{EW}, Y_{EW}, G_{EW} } outputs
 $T \rightarrow$ input

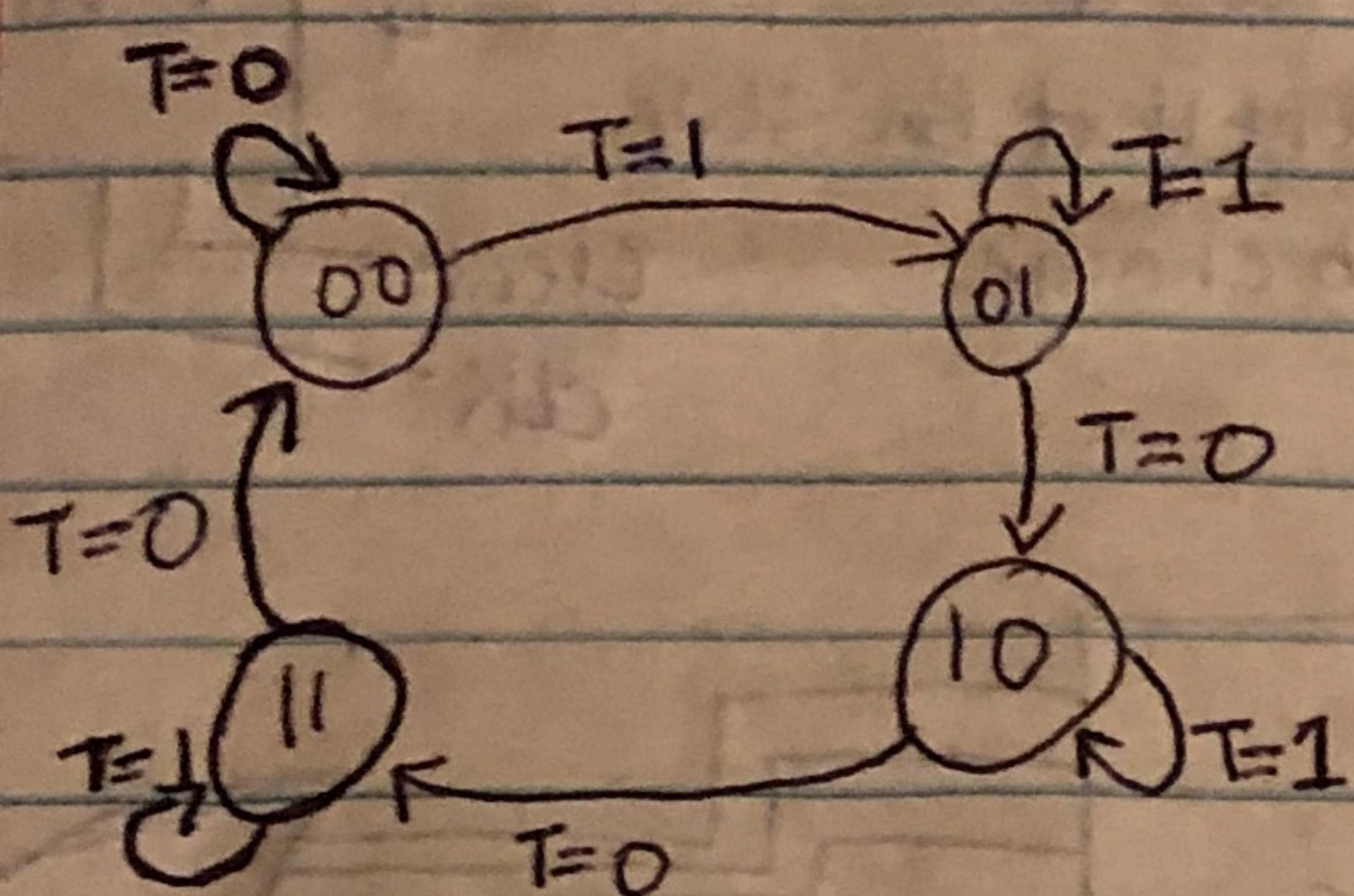$S_0 = T$ NS green on, EW red on
 $S_1 = Ns$ yellow on
 $S_2 = Ns$ red on, EW green on
 $S_3 = EW$ yellow on



| A | B | R_{NS} | Y_{NS} | G_{NS} | R_{EW} | Y_{EW} | G_{EW} |
|---|---|----------|----------|----------|----------|----------|----------|
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 | 0 | 0 | 1 | 0 |

| |
|-----------------|
| $R_{NS} = A$ |
| $Y_{NS} = A'B$ |
| $G_{NS} = A'B'$ |
| $R_{EW} = A'$ |
| $Y_{EW} = AB$ |
| $G_{EW} = AB'$ |

| A | B | T | A_{in} | B_{in} | D_A | D_B |
|---|---|---|-----------------|-----------------|-------|-------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 1 | 0 |
| 1 | 0 | 0 | 1 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 | 1 | 1 |

D_A

| AB | T | 0 | 1 |
|----|---|---|---|
| 00 | 0 | 0 | 0 |
| 01 | 1 | 1 | 0 |
| 11 | 0 | 1 | 1 |
| 10 | 1 | 1 | 1 |

$$D_A = AB' + AT + A'B'T'$$



D_B

| AB | T | 0 | 1 |
|----|---|---|---|
| 00 | 0 | 0 | 1 |
| 01 | 0 | 1 | 1 |
| 11 | 0 | 1 | 1 |
| 10 | 1 | 1 | 0 |

$$D_B = AB'T' + A'T + BT$$

Timer

| Clear | CLK | Load | Count | Function | Count Load |
|-------|-----|------|-------|-----------------------|--|
| 0 | X | X | X | Clear to 0 | |
| 1 | ↑ | 1 | X | Load Inputs | Data-in $\xrightarrow{4}$ 4-bit Binary Counter $\xrightarrow{4}$ |
| 1 | ↑ | 0 | 1 | Count Next Bin. State | |
| 1 | ↑ | 0 | 0 | No change | Clear CLK |

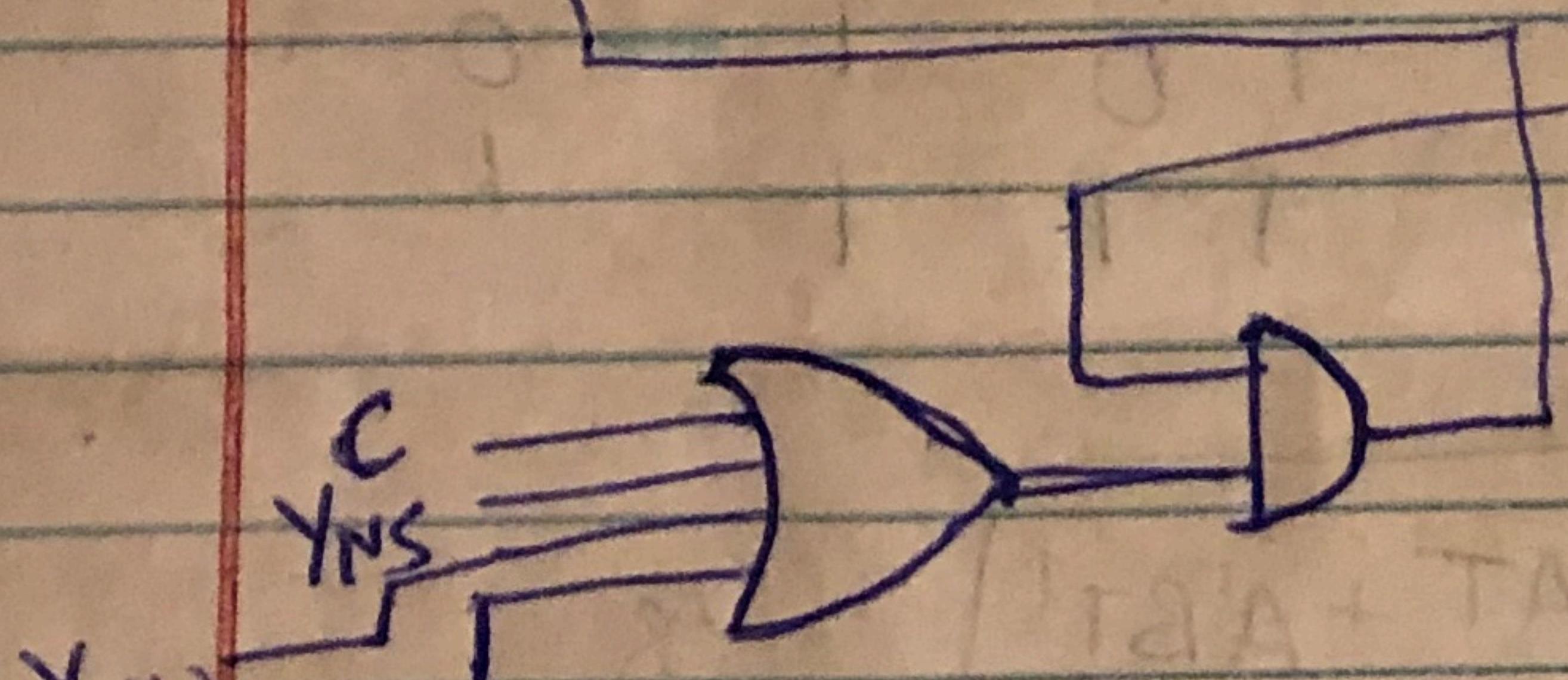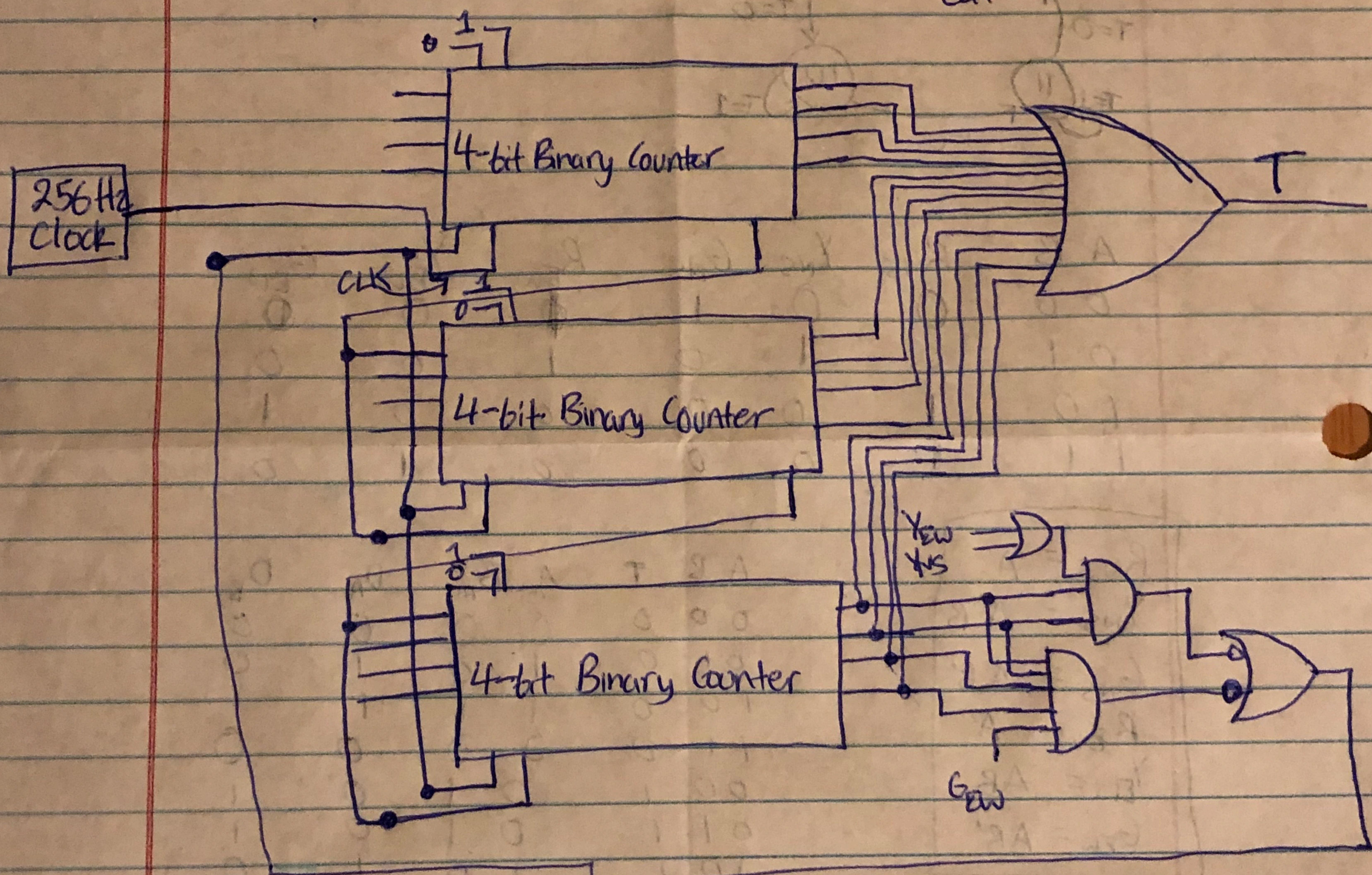

YEW \rightarrow Assume initial inputs is all 0.

Notes: Load = 0, Count = 1. This counter counts up to $256 \cdot 3 = 768 \rightarrow (0111-0000-0000)_2$, or to $256 \cdot 15 = 3840 \rightarrow (1111-0000-0000)_2$.

Hence combinational logic is used around highest 4-bit counter to set clear to 0 (to transition to next state) when 3 sec or 15 sec is achieved depending on outputs (see previous page). T is or of all outputs.